

ELEVATOR USING ARDUINO

DETAILS



CIRCUIT DIAGRAM

HERE, THE PINS OF THE ULN2008 DRIVER ARE CONNECTED TO THE DIGITAL PINS AS FOLLOWS


INT 1-DIGITAL PIN 2

INT 2-DIGITAL PIN 3

INT3-DIGITAL PIN 4

INT4-DIGITAL PIN 5

INT5-DIGITAL PIN 6

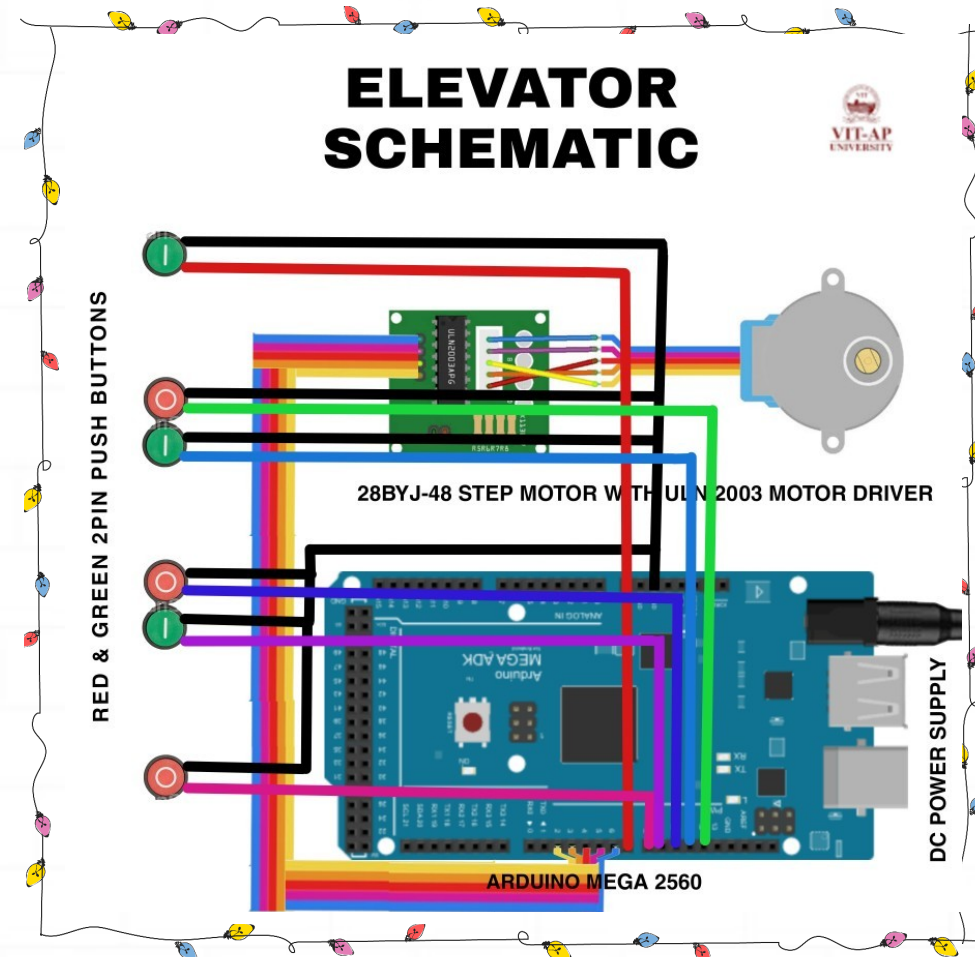

CIRCUIT DIAGRAM

HERE, THE PINS OF THE BUTTONS ARE CONNECTED TO THE DIGITAL PINS&GND AS FOLLWED

BTN 1-DIGITAL PIN 7(GROUND FLOOR)

BTN 2-DIGITAL PIN 8(3rd FLOOR-UP)

BTN3-DIGITAL PIN 9(1st FLOOR-UP)


BTN4-DIGITAL PIN 10(1st FLOOR-DOWN)

BTN5-DIGITAL PIN 11(2nd FLOOR-UP)

BTN6-DIGITAL PIN12(2nd FLOOR-DOWN)

FOR EACH BUTTON THERE ARE 2 PINS IN WHICH ONE PIN IS CONECTED TO GND AND ANOTHER TO THE DIGITAL PIN

ELEVATOR SCHEMATIC

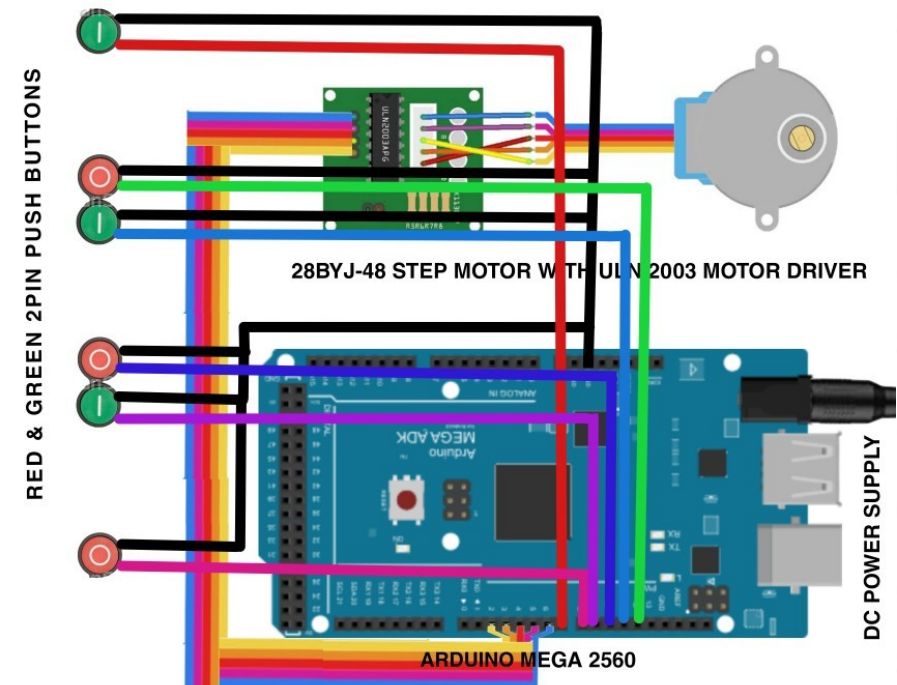


CIRCUIT DIAGRAM



THIS IS THE SCHEMATIC OF THE KART INSIDE THE ELEVATOR, THIS KART HAS A FEATURE LIKE WHEN A PERSON ENTER INTO THE KART THE LIGHTS GET TURNED ON AND WHEN HE LEAVES THE LIGHTS GET TURNED OFF AUTOMATICALLY...WHICH CONSERVES THE POWER A MASSIVE WAY

KART SCHEMATIC

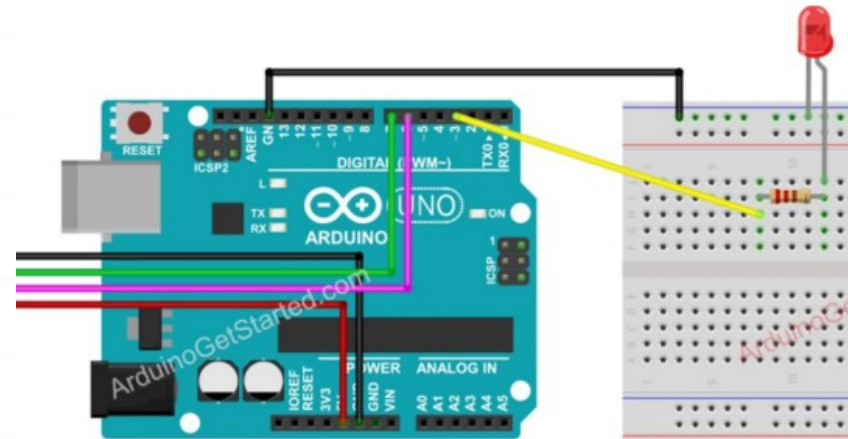



Zoho Show

Untitled Presentation.pdf

(This PDF has been generated using Zoho Show)

To create beautiful presentations, download Zoho Show from Play Store

<https://zoho.to/cy7>